


## CHAPTER 5

© 2016 Pearson Education, Inc.


### 5-1.\*

- a)  $F = (\bar{A} + B)CD$   
 b)  $G = (A + \bar{B})(\bar{C} + D)$

### 5-2.

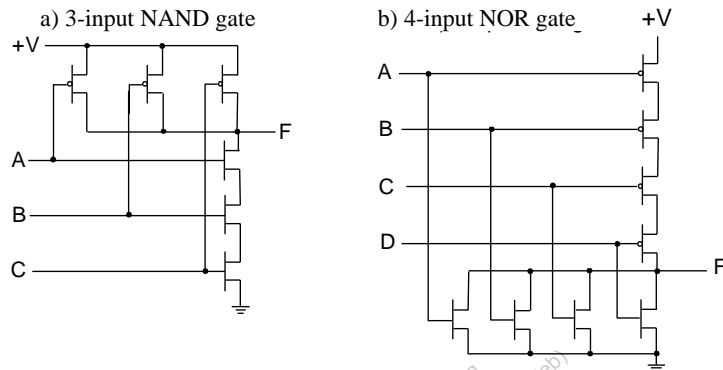


### 5-3.

 

5-4.

a)

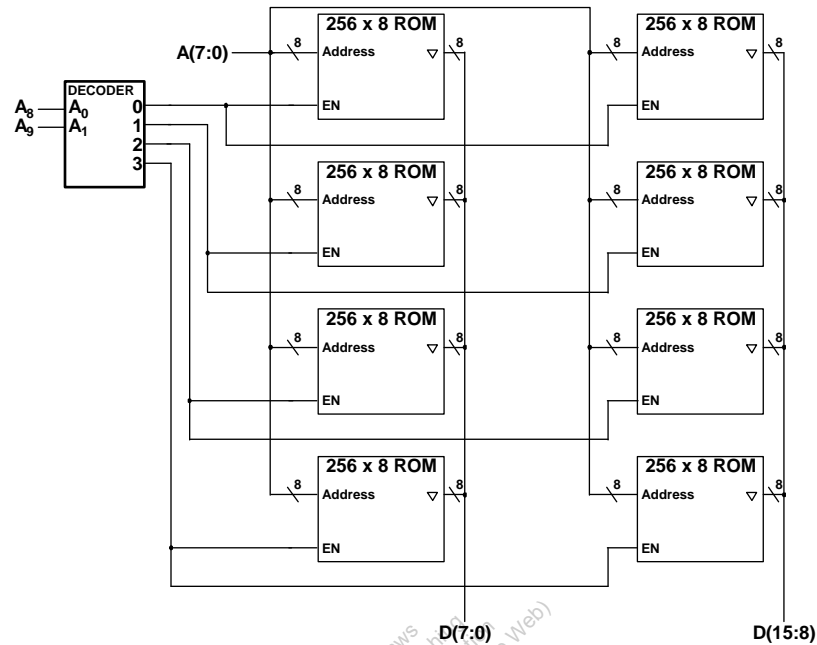

b)  $4K \times 32 / (256 \times 8) = 64$  ROM chips

5-5.\* (Errata: Change "32 X 8" to "64 X 8" ROM)

| IN     | OUT       | IN     | OUT       | IN     | OUT       | IN     | OUT       |
|--------|-----------|--------|-----------|--------|-----------|--------|-----------|
| 000000 | 0000 0000 | 010000 | 0001 0110 | 100000 | 0011 0010 | 110000 | 0100 1000 |
| 000001 | 0000 0001 | 010001 | 0001 0111 | 100001 | 0011 0011 | 110001 | 0100 1001 |
| 000010 | 0000 0010 | 010010 | 0001 1000 | 100010 | 0011 0100 | 110010 | 0101 0000 |
| 000011 | 0000 0011 | 010011 | 0001 1001 | 100011 | 0011 0101 | 110011 | 0101 0001 |
| 000100 | 0000 0100 | 010100 | 0010 0000 | 100100 | 0011 0110 | 110100 | 0101 0010 |
| 000101 | 0000 0101 | 010101 | 0010 0001 | 100101 | 0011 0111 | 110101 | 0101 0011 |
| 000110 | 0000 0110 | 010110 | 0010 0010 | 100110 | 0011 1000 | 110110 | 0101 0100 |
| 000111 | 0000 0111 | 010111 | 0010 0011 | 100111 | 0011 1001 | 110111 | 0101 0101 |
| 001000 | 0000 1000 | 011000 | 0010 0100 | 101000 | 0100 0000 | 111000 | 0101 0110 |
| 001001 | 0000 1001 | 011001 | 0010 0101 | 101001 | 0100 0001 | 111001 | 0101 0111 |
| 001010 | 0001 0000 | 011010 | 0010 0110 | 101010 | 0100 0010 | 111010 | 0101 1000 |
| 001011 | 0001 0001 | 011011 | 0010 0111 | 101011 | 0100 0011 | 111011 | 0101 1001 |
| 001100 | 0001 0010 | 011100 | 0010 1000 | 101100 | 0100 0100 | 111100 | 0110 0000 |
| 001101 | 0001 0011 | 011101 | 0010 1001 | 101101 | 0100 0101 | 111101 | 0110 0001 |
| 001110 | 0001 0100 | 011110 | 0011 0000 | 101110 | 0100 0110 | 111110 | 0110 0010 |
| 001111 | 0001 0101 | 011111 | 0011 0001 | 101111 | 0100 0111 | 111111 | 0110 0011 |


5-6.

- $16 + 16 + 1 = 33$  address bits and  $16 + 1 = 17$  output bits,  $8K \times 17$
- $8 + 8 + 1 + 1 = 18$  address bits and  $8 + 1 = 9$  output bits,  $256K \times 9$
- $4 \times 4 = 16$  address bits and 14 output bits are needed,  $64K \times 14$
- $4 + 4 = 8$  address bits and 8 output bits,  $256 \times 8$

5-7.

| Input |   |   | Output |   |   |   |
|-------|---|---|--------|---|---|---|
| X     | Y | Z | A      | B | C | D |
| 0     | 0 | 0 | 1      | 0 | 0 | 0 |
| 0     | 0 | 1 | 1      | 0 | 0 | 1 |
| 0     | 1 | 0 | 0      | 1 | 1 | 1 |
| 0     | 1 | 1 | 0      | 1 | 0 | 1 |
| 1     | 0 | 0 | 0      | 1 | 0 | 0 |
| 1     | 0 | 1 | 0      | 1 | 0 | 1 |
| 1     | 1 | 0 | 0      | 1 | 1 | 1 |
| 1     | 1 | 1 | 1      | 0 | 0 | 1 |

5-8.

 


By using  $\bar{A}$  instead of A and  $Y\bar{Z}$  instead of Y in D,  $Y\bar{Z}$  can be shared by all four functions. Further, since A is the complement of B, terms  $X\bar{Y}$  and  $\bar{X}Y$  can be shared between A and B. Thus, only four product terms  $Y\bar{Z}$ ,  $X\bar{Y}$ ,  $\bar{X}Y$ , and Z are required. An inversion must be programmed for A.

5-9.

Find the truth table and K-maps:


| X | Y | Z | A | B | C | D | E | F |
|---|---|---|---|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |

 

Implementation of A, D, and E requires only two terms,  $XY$  and  $Y\bar{Z}$ . Straightforward implementation of B, C, and F requires four terms,  $XY$ ,  $XYZ$ ,  $XYZ$ , and Z. By implementing  $\bar{B}$ ,  $\bar{C}$ , and  $\bar{F}$ , only three additional terms  $\bar{X}$ ,  $\bar{X}\bar{Y}$ , and  $\bar{Z}$  are required. So we form the solution using five product terms:  $XY$ ,  $Y\bar{Z}$ ,  $\bar{X}\bar{Y}$ ,  $\bar{X}$ , and  $\bar{Z}$ . The solution is described by the equations given with the six K-maps.

 5-10.


The values given in the four K-maps come from Table 4-4 on page 224.



In this case, shared terms are limited. One such term  $\bar{B}\bar{C}\bar{D}$  is generated in  $\bar{W}$ .

5-11.\*


Assume 3-input OR gates.

 

Each of the equations above is implemented using one 3-input OR gate. Four gates are used.

5-12.


Figure 5-10 uses 3-input OR gates.

 

A, B, and D each require three or fewer product terms so can be implemented with 3-input OR gates. C requires four terms so cannot be implemented with a 3-input OR gate. But because the first PAL device output can be used as an input to implement other functions it can be assigned to A and A can then be used to implement C using just two inputs of a 3-input OR gate.

5-13.

Figure 5-10 uses 3-input OR gates.

 

Straightforward implementation of F requires five prime implicants and of G requires four prime implicants, but only 3 inputs are available on the PAL OR gates. So sum-of-products that can be factored from F and G or both and implemented by the other PAL cells are needed. A single sum of products that will work is  $H = \bar{A}\bar{B}C + B\bar{C}D + BCD$ . The terms of H are shown with dotted lines on the K-maps. Using H:

$$F = H + CD + \bar{A}B$$


$$G = H + \bar{A}B$$

There are other possible functions for H and corresponding results for F and H.

5-14.


- a)  $F(A, B, C) = C(\bar{A}\bar{B} + B) + \bar{C}(\bar{A}B + A)$   
 b)  $F(A, B, C) = C(\bar{A}B + A\bar{B}) + \bar{C}(\bar{A} + B)$

5-15.

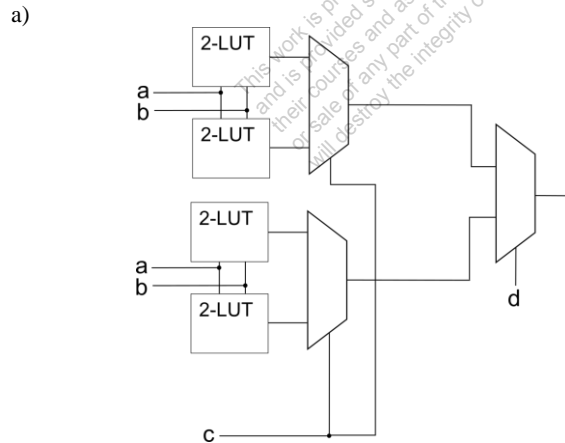

## Problem Solutions – Chapter 5

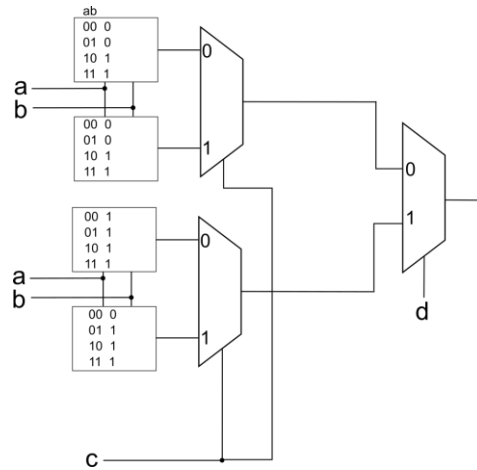- b) Using Shannon's expansion theorem,  $F(A, B, C, D) = D(C(A + B) + \bar{C}(1)) + \bar{D}(C(A) + \bar{C}(A))$ . Then using the 4-LUT from part a, the function can be implemented as:



### 5-16.

Assuming that the upper input of each mux is selected with a 0:

- a) MUX2: 0, MUX3: 1, MUX4: 0
- b) MUX2: 1, MUX3: 1, MUX4: 1
- c) MUX2: 1, MUX3: 1, MUX4: 0

### 5-17.

Invert the b input so that the upper 2-LUT is equal to  $f(a, b) = a \oplus \bar{b}$  and the lower 2-LUT is equal to  $f(a, b) = a\bar{b}$

### 5-18.

The state machine is a Moore machine since the output Z depends only the current state. Using a state assignment of 0 for State0 and 1 for State1, then Z is the same as the state of the flip-flop. Then the configuration bits 0:10 = 1001 0011 111 (assuming that the a input of the 2-LUTs is the most significant bit of the address and that a = in1 and b = in2).